

**Solved Anna University Problems
(NOV/DEC 2010 - NOV/DEC 2019)**

**EC8651-Transmission Lines and RF
Systems**

UNIT 1 - TRANSMISSION LINE THEORY

UNIT 1 - TRANSMISSION LINE THEORY

PROBLEMS

1. Find the characteristic impedance of a line at 1600Hz if $Z_{OC} = 750\angle -30^\circ \Omega$ and $Z_{SC} = 600\angle -20^\circ \Omega$. [EC6503-NOV/DEC 2019](2 Marks), [EC6503-NOV/DEC 2016](2 Marks), [EC6503-APR/MAY 2019](2 Marks)

Solution:

Given: $f = 1600 \text{ Hz}$, $Z_{OC} = 750\angle -30^\circ \Omega$, $Z_{SC} = 600\angle -20^\circ \Omega$

$$Z_o = \sqrt{Z_{OC} \times Z_{SC}}$$

$$Z_o = \sqrt{750 \angle -30^\circ \times 600 \angle -20^\circ}$$

$$\mathbf{Z_o = 670.82 \angle -25^\circ \Omega}$$

2. The following measurement are made on a 25km line at a frequency of 796 Hz. $Z_{SC} = 3220\angle -79.29^\circ \Omega$, $Z_{OC} = 1301\angle 76.67^\circ \Omega$. Determine the primary constants of the line. [EC2305-NOV/DEC 2014](10 Marks)

Solution:

Given: $l = 25\text{Km}$, $f = 796\text{Hz}$, $Z_{SC} = 3220\angle -79.29^\circ \Omega$, $Z_{OC} = 1301\angle 76.67^\circ \Omega$

$$Z_o = \sqrt{Z_{OC} \times Z_{SC}}$$

$$Z_o = \sqrt{1301 \angle 76.67^\circ \times 3220 \angle -79.29^\circ}$$

$$\mathbf{Z_o = 2046.76 \angle -1.31^\circ}$$

$$\tanh \gamma = \sqrt{\frac{Z_{SC}}{Z_{OC}}}$$

$$\tanh \gamma = \sqrt{\frac{3220 \angle -79.29^\circ}{1301 \angle 76.67^\circ}}$$

$$\tanh \gamma = \frac{e^{2\gamma} - 1}{e^{2\gamma} + 1} = 1.5732 \angle -77.98^\circ$$

$$\frac{e^{2\gamma} - 1}{e^{2\gamma} + 1} = 0.3276 - j1.5387$$

$$e^{2\gamma} - 1 = (0.3276 - j1.5387)(e^{2\gamma} + 1)$$

$$e^{2\gamma} - 1 = 0.3276 \times e^{2\gamma} + 0.3276 - j1.5387 \times e^{2\gamma} - j1.5387$$

$$e^{2\gamma} [1 - 0.3276 + j1.5387] = 1 + 0.3276 - j1.5387$$

$$e^{2\gamma} [0.6724 + j1.5387] = 1.3276 - j1.5387$$

$$e^{2\gamma} = \frac{1.3276 - j1.5387}{0.6724 + j1.5387}$$

$$e^{2\gamma} = -0.5231 - j1.0914 = 1.2103 \angle -115.61^\circ$$

$$2\gamma = \ln[1.2103 \angle -115.61^\circ]$$

$$\gamma = \frac{1}{2} \ln[1.2103 \angle -115.61^\circ]$$

Mathematically, $\ln[a \angle b] = \ln a + j b$

$$\gamma = \frac{1}{2} [\ln(1.2103) + j -115.61^\circ]$$

$$\alpha + j\beta = \frac{1}{2} \ln 1.2103 + j \left(\frac{-115.61^\circ}{2} \right)$$

$$\alpha = \frac{1}{2} \ln 1.2103 = 0.0954 \text{ Nepers / Km}$$

$$\alpha = \mathbf{0.0954 \text{ Np/Km}}$$

$$\beta = \left(\frac{-115.61^\circ}{2} \right) = -57.81^\circ / \text{Km} = 1.009 \text{ rad / Km}$$

$$\beta = \mathbf{1.009 \text{ rad/Km}}$$

$$\gamma = \alpha + j\beta = \mathbf{0.0954 + j1.009 = 1.0135 \angle 84.599^\circ}$$

To find Primary Constants:

$$\begin{aligned} R + j\omega L = Z_o P &= 2046.76 \angle -1.31^\circ \times 1.0135 \angle 84.599^\circ \\ &= 242.42 + j2060.18 \end{aligned}$$

Comparing real and imaginary terms,

$$\mathbf{R = 242.42 \text{ ohms/Km}}$$

$$\omega L = 2060.18$$

$$L = \frac{2060.18}{4998.88} = 0.41213 \text{ H / Km}$$

$$\mathbf{L = 0.41213 \text{ H/Km}}$$

Similarly,

$$G + j\omega C = \frac{P}{Z_o} = \frac{1.0135 \angle 84.599^\circ}{2046.76 \angle -1.31^\circ}$$

$$G + j\omega C = 3.533 \times 10^{-5} + j4.939 \times 10^{-4}$$

Comparing real and imaginary terms,

$$\mathbf{G = 3.533 \times 10^{-5} \text{ mho/Km}}$$

$$\omega C = 2.3365 \times 10^{-5}$$

$$C = \frac{4.939 \times 10^{-4}}{4998.88} = 98.8 \text{ nF / Km}$$

$$\mathbf{C = 98.8 \text{ nF/Km}}$$

3. A transmission line has $Z_o = 745 \angle -12^\circ \Omega$ and is terminated in $Z_R = 100 \Omega$. Calculate reflection factor. **[EC6503-APR/MAY 2017](2 Marks)**

Solution:

Given: $Z_o = 745 \angle -12^\circ \Omega$, $Z_R = 100 \Omega$

$$\text{Reflection Factor, } k = \left[\frac{2\sqrt{Z_R Z_o}}{Z_R + Z_o} \right]$$

$$\text{Reflection Factor, } k = \left[\frac{2\sqrt{100 \times 745 \angle -12^\circ}}{100 + 745 \angle -12^\circ} \right]$$

$$\text{Reflection Factor, } k = \left[\frac{545.894 \angle -6^\circ}{843.07 \angle -10.587^\circ} \right]$$

$$\mathbf{\text{Reflection Factor} = 0.6475 \angle 4.587^\circ}$$

4. A transmission line has $Z_o = 745 \angle -12^\circ \Omega$ and is terminated in $Z_R = 100 \Omega$. Calculate reflection loss in dB. **[EC2305-APR/MAY 2011](2 Marks)**

Solution:

Given: $Z_o = 745 \angle -12^\circ \Omega$, $Z_R = 100 \Omega$

$$\text{Reflection loss in dB} = 20 \log \left(\frac{1}{|k|} \right) \text{ dB}$$

$$\text{Reflection Factor, } k = \left[\frac{2\sqrt{Z_R Z_o}}{Z_R + Z_o} \right]$$

$$\text{Reflection Factor, } k = \left[\frac{2\sqrt{100 \times 745 \angle -12^\circ}}{100 + 745 \angle -12^\circ} \right]$$

$$\text{Reflection Factor, } k = \left[\frac{545.894 \angle -6^\circ}{843.07 \angle -10.587^\circ} \right]$$

$$\mathbf{\text{Reflection Factor} = 0.6475 \angle 4.587^\circ}$$

$$\text{Reflection loss in dB} = 20 \log \left(\frac{1}{0.6475} \right) \text{ dB}$$

$$\mathbf{\text{Reflection loss in dB} = 3.7752 \text{ dB}}$$

5. A transmission line has a characteristic impedance of 400Ω and is terminated by a load impedance of $(650-j475) \Omega$. Determine the reflection coefficient. **[EC2305-NOV/DEC 2013](2 Marks)**

Solution:

Given: $Z_O = 400 \Omega$, $Z_R = (650-j475) \Omega$

$$K = \frac{Z_R - Z_O}{Z_R + Z_O} = \frac{(650 - j475) - 400}{(650 - j475) + 400} = \frac{250 - j475}{1050 - j475}$$

$$K = 0.3675 - j0.2861 = 0.4658 \angle -37.9^\circ$$

$$\mathbf{K = 0.4658 \angle -37.9^\circ}$$

6. A transmission line has a characteristic impedance of 600Ω . Determine magnitude of reflection coefficient if the receiving end impedance is $(650-j475) \Omega$. **[EC2305-NOV/DEC 2013](2 Marks)**

Solution:

Given: $Z_O = 600 \Omega$, $Z_R = (650-j475) \Omega$

$$K = \frac{Z_R - Z_O}{Z_R + Z_O} = \frac{(650 - j475) - 600}{(650 - j475) + 600} = \frac{50 - j475}{1250 - j475}$$

$$K = 0.1611 - j0.3188 = 0.3571 \angle -63.18^\circ$$

$$\mathbf{K = 0.3571 \angle -63.18^\circ}$$

7. A transmission line has a characteristic impedance of 300Ω and is terminated in a load impedance of $(150-j150) \Omega$. Determine the reflection coefficient. **[EC2305-APR/MAY 2014](2 Marks)**

Solution:

Given: $Z_O = 300 \Omega$, $Z_R = (150-j150) \Omega$

$$K = \frac{Z_R - Z_O}{Z_R + Z_O} = \frac{(150 - j150) - 300}{(150 - j150) + 300} = \frac{-150 - j150}{450 - j150}$$

$$K = -0.2 - j0.4 = 0.4472 \angle -116.57^\circ$$

$$\mathbf{K = 0.4472 \angle -116.57^\circ}$$

8. Find the reflection coefficient of a 50 ohm line when it is terminated by a load impedance of $60+j40 \text{ ohm}$. **[EC6503-NOV/DEC 2015](2 Marks), [EC2305-NOV/DEC 2015](2 Marks)[EC2305-APR/MAY 2013](2 Marks)**

Solution:

Given: $Z_O = 50 \Omega$, $Z_R = (60+j40) \Omega$

$$K = \frac{Z_R - Z_O}{Z_R + Z_O} = \frac{(60 + j40) - 50}{(60 + j40) + 50} = \frac{10 + j40}{110 + j40}$$

$$K = 0.197 + j0.29197 = 0.3523 \angle 55.98^\circ$$

$$\mathbf{K = 0.3523 \angle 55.98^\circ}$$

9. The constant of a transmission line are $R=6\Omega/\text{Km}$, $L=2.2\text{mH}/\text{Km}$, $C=0.005\mu\text{F}/\text{Km}$ and $G=0.25 \times 10^{-3} \text{ mho}/\text{Km}$, Calculate the characteristic impedance, attenuation constant and phase constant at 1000 Hz.

[EC6503-NOV/DEC 2019](6 Marks) [EC6503-APR/MAY 2019](6 Marks), [EC2305-APR/MAY 2014](8 Marks)

Solution:

Given: $R=6\Omega/\text{Km}$, $L=2.2\text{mH}/\text{Km}$, $C=0.005\mu\text{F}/\text{Km}$ and $G=0.25 \times 10^{-3} \text{ mho}/\text{Km}$, $f=1000 \text{ Hz}$

$$\omega = 2\pi f = 2 \times 3.14 \times 1000 = 6280$$

The characteristic impedance is given by,

$$Z_o = \sqrt{\frac{R + j\omega L}{G + j\omega C}}$$

$$Z_o = \sqrt{\frac{6 + j(6280)(2.2 \times 10^{-3})}{0.25 \times 10^{-3} + j(6280)(0.005 \times 10^{-6})}}$$

$$Z_o = \sqrt{\frac{6 + j13.816}{0.25 \times 10^{-3} + j3.14 \times 10^{-5}}} = \sqrt{\frac{15.063 \angle 66.526^\circ}{2.52 \times 10^{-4} \angle 7.159^\circ}}$$

$$Z_o = \frac{3.881}{0.0159} \angle (66.526^\circ - 7.159^\circ) / 2$$

$$\mathbf{Z_o = 244.088 \angle 29.68^\circ}$$

The propagation constant is given by,

$$P = \gamma = \sqrt{(R + j\omega L)(G + j\omega C)}$$

$$P = \gamma = \sqrt{(6 + j(6280)(2.2 \times 10^{-3})) \times (0.25 \times 10^{-3} + j(6280)(0.005 \times 10^{-6}))}$$

$$P = \gamma = \sqrt{(6 + j13.816) \times (0.25 \times 10^{-3} + j3.14 \times 10^{-5})}$$

$$P = \gamma = \sqrt{15.063 \angle 66.526^\circ \times 2.52 \times 10^{-4} \angle 7.159^\circ}$$

$$P = \gamma = \sqrt{15.063 \times 2.52 \times 10^{-4} \angle (7.159^\circ + 66.526^\circ)}$$

$$P = \gamma = \alpha + j\beta = 0.0616 \angle 36.843^\circ \text{ (Or) } 0.0493 + j0.0369$$

attenuation constant, $\alpha = 0.0493$

and phase constant, $\beta = 0.0369$

10. A transmission line has a characteristic impedance of $(683-j138)$ ohm. the propagation constant is $(0.0074+j0.0356)$ per Km. Determine the values of R and L of this line if the frequency is 1000Hz.

[EC2305-APR/MAY 2014](6 Marks)

Solution:

Given: $Z_o = 683-j138\Omega$, $\gamma = P = 0.0074+j0.0356$, $f=1000\text{Hz}$

$$\omega = 2\pi f = 2 \times 3.14 \times 1000 = 6280$$

$$\begin{aligned} R+j\omega L &= Z_o P = (683-j138) \times (0.0074+j0.0356) \\ &= 9.967+j23.2936 \end{aligned}$$

Comparing real and imaginary terms,

R = 9.967 ohms/Km

$$\omega L = 23.2936$$

$$L = \frac{23.2936}{6280} = 3.7092 \text{ mH / Km}$$

L=3.7092 mH/Km

11. A Communication line has $L=3.67 \text{ mH/Km}$, $G=0.08 \times 10^{-6} \text{ mho/Km}$, $C=0.0083 \mu\text{F/Km}$ and $R=10.4 \Omega/\text{Km}$. Determine the characteristic impedance, propagation constant, phase constant, velocity of propagation, sending end current and receiving end current for a given frequency $f=1000 \text{ Hz}$. sending end voltage is 1V and transmission line length is 100Kms.

[EC6503-NOV/DEC 2016] (16 Marks) [EC6503-APR/MAY 2018](13 Marks)

Solution:

Given: $E_s = 1\text{V}$, $f=1000 \text{ Hz}$, $l=100 \text{ Km}$, $R=10.4 \Omega/\text{Km}$, $L = 0.00367\text{H/Km}$, $G = 0.08 \times 10^{-6} \text{ mho/Km}$, $C = 0.0083 \mu\text{F/Km}$

$$\omega = 2\pi f = 2 \times 3.14 \times 1000 = 6280$$

The characteristic impedance is given by,

$$Z_o = \sqrt{\frac{Z}{Y}} = \sqrt{\frac{R + j\omega L}{G + j\omega C}}$$

$$Z = R + j\omega L = 10.4 + j(6280)(.00367) = 25.285 \angle 65.71^\circ$$

$$Y = G + j\omega C = 0.08 \times 10^{-6} + j(6280)(0.0083 \times 10^{-6}) = 5.212 \times 10^{-5} \angle 89.91^\circ$$

$$Z_o = \sqrt{\frac{25.285 \angle 65.71^\circ}{5.212 \times 10^{-5} \angle 89.91^\circ}}$$

$$Z_o = \frac{5.028}{7.2194 \times 10^{-3}} \angle (65.71^\circ - 89.91^\circ) / 2$$

$Z_o = 696.46 \angle -12.1^\circ \Omega$

The propagation constant is given by,

$$P = \gamma = \sqrt{ZY} = \sqrt{(R + j\omega L)(G + j\omega C)}$$

$$P = \gamma = \sqrt{25.285 \angle 65.71^\circ \times 5.212 \times 10^{-5} \angle 89.91^\circ}$$

$$P = \gamma = \sqrt{1.319 \times 10^{-3} \angle (65.71^\circ + 89.91^\circ)}$$

$$P = \gamma = \alpha + j\beta = 0.0363 \angle 77.81^\circ \text{ (Or) } 7.6649 \times 10^{-3} + j0.0355$$

attenuation constant, $\alpha = 7.6649 \times 10^{-3} \text{ Np/Km}$

and phase constant, $\beta = 0.0355 \text{ rad/Km}$

The velocity of propagation is given by,

$$v_p = \frac{\omega}{\beta}$$

$$v_p = \frac{6280}{0.0355} = 1.769 \times 10^5 \text{ Km/sec}$$

$$\lambda = \frac{2\pi}{\beta} = \frac{2\pi}{0.0355} = 176.99 \text{ m}$$

NOTE: Z_R value is not given in the question. so, assume the line is perfectly matched line to proceed further. i.e., $Z_R = Z_0$, $Z_S = Z_0$

$$I_S = \frac{E_g}{Z_g + Z_{in}} = \frac{E_g}{Z_g + Z_S}$$

$$I_S = \frac{1}{0 + 696.46 \angle -12.1^\circ} = 1.4358 \times 10^{-3} \angle 12.1^\circ \text{ A}$$

$$\mathbf{I_S = 1.4358 \times 10^{-3} \angle 12.1^\circ}$$

We know that,

$$I = \frac{I_R}{2} \left(\frac{Z_R + Z_0}{Z_0} \right) \left[e^{\sqrt{ZY}s} - \frac{(Z_R - Z_0)}{(Z_R + Z_0)} e^{-\sqrt{ZY}s} \right]$$

At sending end, $s=l$, and put $K=0$, because $Z_R = Z_0$.

$$I_S = I_R e^{\sqrt{ZY}l}$$

$$I_R = I_S e^{-\sqrt{ZY}l}$$

$$e^{-\sqrt{ZY}l} = e^{-\gamma l} = e^{-(7.6649 \times 10^{-3} + j0.0355) \times 100} = e^{-0.76649} \angle 203.4^\circ$$

$$e^{-\sqrt{ZY}l} = 0.4646 \angle 203.4^\circ$$

$$\therefore I_R = 1.4358 \times 10^{-3} \angle 12.1^\circ \times 0.4646 \angle 203.4^\circ$$

$$\mathbf{I_R = 6.671 \times 10^{-4} \angle -144.5^\circ \text{ A}}$$

12. A Parallel wire transmission line is having the following line parameters at 5 KHz. Series resistance ($R = 2.59 \times 10^{-3} \Omega / m$), Series inductance ($L = 2 \mu H / m$), shunt conductance ($G = 0 \Omega / m$) and capacitance between conductors ($C = 5.56 \text{ pF} / m$). Find the characteristic impedance, attenuation constant ($\alpha \text{ Np} / m$), Phase shift constant ($\beta \text{ rad} / m$), velocity of propagation and wavelength.
[EC6503-NOV/DEC 2015](10 Marks), [EC2305-NOV/DEC 2015](10 Marks)

Solution:

Given: $f = 5 \text{ KHz}$, $R = 2.59 \times 10^{-3} \Omega / m$, $L = 2 \mu H / m$, $G = 0 \text{ mho} / m$, $C = 5.56 \text{ pF} / m$

$$\omega = 2\pi f = 2 \times 3.14 \times 5000 = 31400$$

The characteristic impedance is given by,

$$Z_o = \sqrt{\frac{Z}{Y}} = \sqrt{\frac{R + j\omega L}{G + j\omega C}}$$

$$Z = R + j\omega L = 2.59 \times 10^{-3} + j(31400)(2 \times 10^{-6}) = 0.0629 \angle 87.64^\circ$$

$$Y = G + j\omega C = j(31400)(5.56 \times 10^{-12}) = 1.746 \times 10^{-7} \angle 90^\circ$$

$$Z_o = \sqrt{\frac{0.0629 \angle 87.64^\circ}{1.746 \times 10^{-7} \angle 90^\circ}}$$

$$Z_o = \frac{0.2508}{4.1785 \times 10^{-4}} \angle (87.64^\circ - 90^\circ) / 2$$

$$\mathbf{Z_o = 600.21 \angle -1.18^\circ \Omega}$$

The propagation constant is given by,

$$P = \gamma = \sqrt{ZY} = \sqrt{(R + j\omega L)(G + j\omega C)}$$

$$P = \gamma = \sqrt{0.0629 \angle 87.64^\circ \times 1.746 \times 10^{-7} \angle 90^\circ}$$

$$P = \gamma = \sqrt{1.09823 \times 10^{-8} \angle (87.64^\circ + 90^\circ)}$$

$$P = \gamma = \alpha + j\beta = 1.048 \times 10^{-4} \angle 88.82^\circ \text{ (Or) } 2.1582 \times 10^{-6} + j1.04778 \times 10^{-4}$$

attenuation constant, $\alpha = 2.158 \times 10^{-6} \text{ Np} / m$

and phase constant, $\beta = 104.778 \times 10^{-6} \text{ rad} / m$

The velocity of propagation is given by,

$$v_p = \frac{\omega}{\beta}$$

$$v_p = \frac{31400}{104.778 \times 10^{-6}} = 2.997 \times 10^8 \text{ m} / \text{sec}$$

$$\lambda = \frac{2\pi}{\beta} = \frac{2\pi}{104.778 \times 10^{-6}} = 59.94 \times 10^3 \text{ m}$$

13. A 2 meter long transmission line with characteristics impedance of $60+j40$ ohm is operating at $\omega = 10^6$ rad / sec has attenuation constant of 0.921 Np/m and phase shift constant of 0 rad /m. If the line is terminated by a load of $20+j50$ ohm, determine the input impedance of this line.

[EC6503-NOV/DEC 2015](6 Marks), [EC6503-APR/MAY 2017](8 Marks), [EC2305-NOV/DEC 2015](6 Marks), [EC2305-APR/MAY 2019](8 Marks)

Solution:

Given: $l = 2\text{m}$, $Z_o = 60+j40\Omega$, $\omega = 10^6$ rad/sec, $\alpha = 0.921$ Np/m, $\beta = 0$ rad /m,
 $Z_R = 20+j50 \Omega$

Reflection Coefficient, K

$$K = \frac{Z_R - Z_o}{Z_R + Z_o}$$

$$K = \frac{(20 + j50) - (60 + j40)}{(20 + j50) + (60 + j40)} = -0.1586 + j0.30345 = 0.3424 \angle 117.6^\circ$$

$$\mathbf{K = 0.3424 \angle 117.6^\circ}$$

$$e^{\gamma l} = e^{(\alpha + j\beta)l} = e^{\alpha l} \angle \beta l = e^{(0.921)(2)} \angle (0)(2)$$

$$e^{\gamma l} = e^{1.842}$$

$$\mathbf{e^{\gamma l} = 6.3091 \angle 0^\circ}$$

$$e^{-\gamma l} = e^{-(\alpha + j\beta)l} = e^{-\alpha l} \angle -\beta l = e^{-(0.921)(2)} \angle -(0)(2)$$

$$e^{-\gamma l} = e^{-1.842}$$

$$\mathbf{e^{-\gamma l} = 0.1585 \angle 0^\circ}$$

$$Z_s = Z_o \left\{ \frac{e^{\gamma l} + K e^{-\gamma l}}{e^{\gamma l} - K e^{-\gamma l}} \right\}$$

$$Z_s = 72.11 \angle 33.69^\circ \left\{ \frac{6.3091 + (0.3424 \angle 117.6^\circ)(0.1585)}{6.3091 - (0.3424 \angle 117.6^\circ)(0.1585)} \right\}$$

$$Z_s = 72.11 \angle 33.69^\circ \left\{ \frac{6.3091 + 0.0543 \angle 117.6^\circ}{6.3091 - 0.0543 \angle 117.6^\circ} \right\}$$

$$Z_s = 72.11 \angle 33.69^\circ \left\{ \frac{6.284 \angle 0.4387^\circ}{6.3344 \angle -0.4353^\circ} \right\}$$

$$Z_s = 72.11 \angle 33.69^\circ \{ 0.9920 \angle 0.8740^\circ \}$$

$$\mathbf{Z_s = 71.54 \angle 34.56^\circ \Omega}$$

14. A generator of 1V, 1000 Hz, supplies power to a 100 Km open wire line terminated in Z_O and having following parameters $R = 10.4$ ohm per Km, $L = 0.00367$ Henry per Km, $G = 0.8 \times 10^{-6}$ mho per Km, $C = 0.00835 \mu\text{F}$ per Km. Calculate Z_O , α , β , λ , v . also find the received power.

[EC6503-MAY/JUN 2016](16 Marks), [EC6503-APR/MAY 2016](16 Marks), [EC6503-APR/MAY 2015](16 Marks)

Solution:

Given: $E_g = 1\text{V}$, $f=1000$ Hz, $l=100$ Km, when $Z_R = Z_O$ then $Z_S = Z_O$, $R=10.4 \Omega/\text{Km}$, $L = 0.00367\text{H}/\text{Km}$, $G = 0.8 \times 10^{-6}$ mho/Km, $C = 0.00835 \mu\text{F}/\text{Km}$

$$\omega = 2\pi f = 2 \times 3.14 \times 1000 = 6280$$

The characteristic impedance is given by,

$$Z_O = \sqrt{\frac{Z}{Y}} = \sqrt{\frac{R + j\omega L}{G + j\omega C}}$$

$$Z = R + j\omega L = 10.4 + j(6280)(.00367) = 25.285 \angle 65.71^\circ$$

$$Y = G + j\omega C = 0.8 \times 10^{-6} + j(6280)(0.00835 \times 10^{-6}) = 5.244 \times 10^{-5} \angle 89.13^\circ$$

$$Z_O = \sqrt{\frac{25.285 \angle 65.71^\circ}{5.244 \times 10^{-5} \angle 89.13^\circ}}$$

$$Z_O = \frac{5.028}{7.24 \times 10^{-3}} \angle (65.71^\circ - 89.13^\circ) / 2$$

$$\mathbf{Z_O = 694.48 \angle -11.71^\circ \Omega}$$

The propagation constant is given by,

$$P = \gamma = \sqrt{ZY} = \sqrt{(R + j\omega L)(G + j\omega C)}$$

$$P = \gamma = \sqrt{25.285 \angle 65.71^\circ \times 5.244 \times 10^{-5} \angle 89.13^\circ}$$

$$P = \gamma = \sqrt{1.326 \times 10^{-3} \angle (65.71^\circ + 89.13^\circ)}$$

$$P = \gamma = \alpha + j\beta = 0.0364 \angle 77.42^\circ \text{ (Or) } 7.928 \times 10^{-3} + j0.0355$$

attenuation constant, $\alpha = 7.928 \times 10^{-3} \text{ Np/Km}$

and phase constant, $\beta = 0.0355 \text{ rad/Km}$

The velocity of propagation is given by,

$$v_p = \frac{\omega}{\beta}$$

$$v_p = \frac{6280}{0.0355} = 1.769 \times 10^5 \text{ Km/sec}$$

$$\lambda = \frac{2\pi}{\beta} = \frac{2\pi}{0.0355} = 176.99 \text{ m}$$

$$I_S = \frac{E_g}{Z_g + Z_{in}} = \frac{E_g}{Z_g + Z_S}$$

$$I_S = \frac{1}{0 + 694.48 \angle -11.71^\circ} = 1.4399 \times 10^{-3} \angle 11.71^\circ \text{ A}$$

$$\mathbf{I_S = 1.4399 \times 10^{-3} \angle 11.71^\circ}$$

$$E_S = I_S \times Z_S$$

$$E_S = 1.4399 \times 10^{-3} \angle 11.71^\circ \times (694.48 \angle -11.71^\circ)$$

$$\mathbf{E_S = 1 \text{ V}}$$

We know that,

$$I = \frac{I_R}{2} \left(\frac{Z_R + Z_o}{Z_o} \right) \left[e^{\sqrt{ZY}s} - \frac{(Z_R - Z_o)}{(Z_R + Z_o)} e^{-\sqrt{ZY}s} \right]$$

At sending end, $s=1$, and put $K=0$, because $Z_R = Z_O$.

$$I_S = I_R e^{\sqrt{ZY}1}$$

$$I_R = I_S e^{-\sqrt{ZY}1}$$

$$e^{-\sqrt{ZY}1} = e^{-\gamma l} = e^{-(7.928 \times 10^{-3} + j0.0355) \times 100} = e^{-0.7928} \angle 203.4^\circ$$

$$e^{-\sqrt{ZY}1} = 0.4526 \angle 203.4^\circ$$

$$\therefore I_R = 1.4399 \times 10^{-3} \angle 11.71^\circ \times 0.4526 \angle 203.4^\circ$$

$$\mathbf{I_R = 6.517 \times 10^{-4} \angle -144.89^\circ}$$

$$E_R = I_R \times Z_R = 6.517 \times 10^{-4} \angle -144.89^\circ \times (694.48 \angle -11.71^\circ)$$

$$\mathbf{E_R = 0.4526 \angle -156.6^\circ \text{ V}}$$

$$P_S = |E_S| \cdot |I_S| \cdot \cos(E_S \wedge I_S)$$

$$P_S = 1 \times 1.4399 \times 10^{-3} \times \cos(11.71)$$

$$\mathbf{P_S = 1.4099 \times 10^{-3} \text{ W}}$$

$$\text{and } P_R = |E_R| \cdot |I_R| \cdot \cos(E_R \wedge I_R)$$

$$P_R = 0.4526 \times 6.517 \times 10^{-4} \cos(-11.71)$$

$$\mathbf{P_R = 0.28882 \times 10^{-3} \text{ W}}$$

15. A generator of 1V, 1000 cycles, supplies power to a 100 mile open wire line terminated in Z_O and having following parameters: Series resistance $R = 10.4$ ohm/ mile, Series inductance $L = 0.00367$ H/mile, Shunt conductance $G = 0.8 \times 10^{-6}$ mho/ mile, and capacitance between conductors $C = 0.00835$ μ F/mile. Find the characteristic impedance, Propagation constant, attenuation constant, phase shift constant, velocity of propagation and wavelength.
[EC6503-APR/MAY 2017](6 Marks)

Solution:

Given: $E_g = 1V$, $f=1000$ cycles = 1000 Hz, $l=100$ mile, when $Z_R = Z_O$ then $Z_S = Z_O$, $R=10.4 \Omega$ / mile, $L = 0.00367H$ / mile, $G = 0.8 \times 10^{-6}$ mho/ mile, $C = 0.00835 \mu F$ / mile

$$\omega = 2\pi f = 2 \times 3.14 \times 1000 = 6280$$

The characteristic impedance is given by,

$$Z_o = \sqrt{\frac{Z}{Y}} = \sqrt{\frac{R + j\omega L}{G + j\omega C}}$$

$$Z = R + j\omega L = 10.4 + j(6280)(0.00367) = 25.285 \angle 65.71^\circ$$

$$Y = G + j\omega C = 0.8 \times 10^{-6} + j(6280)(0.00835 \times 10^{-6}) = 5.244 \times 10^{-5} \angle 89.13^\circ$$

$$Z_o = \sqrt{\frac{25.285 \angle 65.71^\circ}{5.244 \times 10^{-5} \angle 89.13^\circ}}$$

$$Z_o = \frac{5.028}{7.24 \times 10^{-3}} \angle (65.71^\circ - 89.13^\circ) / 2$$

$$\mathbf{Z_o = 694.48 \angle -11.71^\circ \Omega}$$

The propagation constant is given by,

$$P = \gamma = \sqrt{ZY} = \sqrt{(R + j\omega L)(G + j\omega C)}$$

$$P = \gamma = \sqrt{25.285 \angle 65.71^\circ \times 5.244 \times 10^{-5} \angle 89.13^\circ}$$

$$P = \gamma = \sqrt{1.326 \times 10^{-3} \angle (65.71^\circ + 89.13^\circ)}$$

$$P = \gamma = \alpha + j\beta = 0.0364 \angle 77.42^\circ \text{ (Or) } 7.928 \times 10^{-3} + j0.0355$$

attenuation constant, $\alpha = 7.928 \times 10^{-3}$ Np/Km

and phase constant, $\beta = 0.0355$ rad/Km

The velocity of propagation is given by,

$$v_p = \frac{\omega}{\beta}$$

$$v_p = \frac{6280}{0.0355} = 1.769 \times 10^5 \text{ Km/sec}$$

$$\lambda = \frac{2\pi}{\beta} = \frac{2\pi}{0.0355} = 176.99 \text{ m}$$

16. A generator of 1V, 1KHz, supplies power to a 100 Km open wire line terminated in 200 Ω resistance. The line parameters are $R = 10 \Omega/\text{Km}$, $L = 3.8\text{mH}/\text{Km}$, $G = 1 \times 10^{-6} \text{ mho}/\text{Km}$, $C = 0.0085 \mu\text{F}/\text{Km}$. Calculate Z_o , α , β , λ , v . also find the received power. **[EC2305-NOV/DEC 2018](16 Marks)**

Solution:

Given: $E_g = 1\text{V}$, $f = 1000 \text{ Hz}$, $l = 100 \text{ Km}$, $Z_R = 200 \Omega$, $R = 10 \Omega/\text{Km}$, $L = 3.8\text{mH}/\text{Km}$, $G = 1 \times 10^{-6} \text{ mho}/\text{Km}$, $C = 0.0085 \mu\text{F}/\text{Km}$

$$\omega = 2\pi f = 2 \times 3.14 \times 1000 = 6280$$

The characteristic impedance is given by,

$$Z_o = \sqrt{\frac{Z}{Y}} = \sqrt{\frac{R + j\omega L}{G + j\omega C}}$$

$$Z = R + j\omega L = 10 + j(6280)(3.8 \times 10^{-3}) = 25.87 \angle 67.26^\circ$$

$$Y = G + j\omega C = 1 \times 10^{-6} + j(6280)(0.0085 \times 10^{-6}) = 5.339 \times 10^{-5} \angle 88.93^\circ$$

$$Z_o = \sqrt{\frac{25.87 \angle 67.26^\circ}{5.339 \times 10^{-5} \angle 88.93^\circ}}$$

$$Z_o = \frac{5.086}{7.307 \times 10^{-3}} \angle (67.26^\circ - 88.93^\circ) / 2$$

$$\mathbf{Z_o = 696.06 \angle -10.84^\circ \Omega}$$

The propagation constant is given by,

$$P = \gamma = \sqrt{ZY} = \sqrt{(R + j\omega L)(G + j\omega C)}$$

$$P = \gamma = \sqrt{25.87 \angle 67.26^\circ \times 5.339 \times 10^{-5} \angle 88.93^\circ}$$

$$P = \gamma = \sqrt{1.3812 \times 10^{-3} \angle (67.26^\circ + 88.93^\circ)}$$

$$P = \gamma = \alpha + j\beta = 0.03716 \angle 78.095^\circ \text{ (Or) } 7.6657 \times 10^{-3} + j0.03636$$

attenuation constant, $\alpha = 7.6657 \times 10^{-3} \text{ Np/Km}$

and phase constant, $\beta = 0.03636 \text{ rad/Km}$

The velocity of propagation is given by,

$$v_p = \frac{\omega}{\beta}$$

$$v_p = \frac{6280}{0.03636} = 1.727 \times 10^5 \text{ Km/sec}$$

$$\lambda = \frac{2\pi}{\beta} = \frac{2\pi}{0.03636} = 172.72 \text{ m}$$

Reflection Coefficient, K

$$K = \frac{Z_R - Z_o}{Z_R + Z_o}$$

$$K = \frac{200 - 696.06 \angle -10.84^\circ}{200 + 696.06 \angle -10.84^\circ} = -0.557 + j0.0656 = 0.5609 \angle 173.28^\circ$$

$$\mathbf{K=0.5609 \angle 173.28^\circ}$$

$$e^{\gamma l} = e^{(\alpha + j\beta)l} = e^{\alpha l} \angle \beta l = e^{(7.6657 \times 10^{-3})(100)} \angle (0.03636)(100)$$

$$e^{\gamma l} = e^{(7.6657 \times 10^{-3})(100)} \angle (0.03636)(100) \text{ rad}$$

$$e^{\gamma l} = e^{0.76657} \angle 208.3^\circ$$

$$\mathbf{e^{\gamma l} = 2.1524 \angle 208.3^\circ}$$

$$e^{-\gamma l} = e^{-(\alpha + j\beta)l} = e^{-\alpha l} \angle -\beta l = e^{-(7.6657 \times 10^{-3})(100)} \angle -(0.03636)(100)$$

$$e^{-\gamma l} = e^{-(7.6657 \times 10^{-3})(100)} \angle -(0.03636)(100) \text{ rad}$$

$$e^{-\gamma l} = e^{-0.76657} \angle -208.3^\circ$$

$$\mathbf{e^{-\gamma l} = 0.4646 \angle -208.3^\circ}$$

$$Z_s = Z_o \left\{ \frac{e^{\gamma l} + K e^{-\gamma l}}{e^{\gamma l} - K e^{-\gamma l}} \right\}$$

$$Z_s = 696.06 \angle -10.84^\circ \left\{ \frac{2.1524 \angle 208.3^\circ + (0.5609 \angle 173.28^\circ)(0.4646 \angle -208.3^\circ)}{2.1524 \angle 208.3^\circ - (0.5609 \angle 173.28^\circ)(0.4646 \angle -208.3^\circ)} \right\}$$

$$Z_s = 696.06 \angle -10.84^\circ \left\{ \frac{2.1524 \angle 208.3^\circ + 0.2606 \angle -35.02^\circ}{2.1524 \angle 208.3^\circ - 0.2606 \angle -35.02^\circ} \right\}$$

$$Z_s = 696.06 \angle -10.84^\circ \left\{ \frac{2.0487 \angle -145.17^\circ}{2.2813 \angle -157.56^\circ} \right\}$$

$$Z_s = 696.06 \angle -10.84^\circ \times 0.8980 \angle 12.39^\circ$$

$$\mathbf{Z_s = 625.08 \angle 1.548^\circ}$$

$$I_s = \frac{E_g}{Z_g + Z_{in}} = \frac{E_g}{Z_g + Z_s}$$

$$I_s = \frac{1}{0 + 625.08 \angle 1.548^\circ} = 1.5992 \times 10^{-3} \angle -1.548^\circ \text{ A}$$

$$\mathbf{I_s = 1.5992 \times 10^{-3} \angle -1.548^\circ}$$

$$E_s = I_s \times Z_s$$

$$E_s = 1.5992 \times 10^{-3} \angle -1.548^\circ \times 625.08 \angle 1.548^\circ$$

$$\mathbf{E_s = 1 \angle -3.4484 \times 10^{-4} \text{ V}}$$

We know that,

$$I = \frac{I_R}{2} \left(\frac{Z_R + Z_o}{Z_o} \right) \left[e^{\sqrt{ZY}s} - \frac{(Z_R - Z_o)}{(Z_R + Z_o)} e^{-\sqrt{ZY}s} \right]$$

At sending end, s=l, as s is measured from the receiving end.

$$I_s = \frac{I_R}{2} \left(\frac{Z_R + Z_o}{Z_o} \right) \left[e^{\sqrt{ZYI}} - K e^{-\sqrt{ZYI}} \right]$$

$$Z_R + Z_o = 893.28 \angle -8.427^\circ$$

$$K e^{\sqrt{ZYI}} = 0.5609 \angle 173.28^\circ \times 2.1524 \angle 208.3^\circ$$

$$K e^{\sqrt{ZYI}} = 1.2073 \angle 21.58^\circ$$

$$1.5992 \times 10^{-3} \angle -1.548^\circ = \frac{I_R}{2} \left(\frac{893.28 \angle -8.427^\circ}{696.06 \angle -10.84^\circ} \right) \left[2.1524 \angle 208.3^\circ - 1.2073 \angle 21.58^\circ \right]$$

$$1.5992 \times 10^{-3} \angle -1.548^\circ = \frac{I_R}{2} (1.2833 \angle 2.413^\circ) [3.354 \angle -154.11^\circ]$$

$$1.5992 \times 10^{-3} \angle -1.548^\circ = I_R \times 2.1523 \angle -151.70^\circ$$

$$I_R = 7.43 \times 10^{-4} \angle 150.15^\circ$$

$$E_R = I_R \times Z_R = 7.43 \times 10^{-4} \angle 150.15^\circ \times 200 = 0.1486 \angle 150.153^\circ$$

$$E_R = 0.1486 \angle 150.15^\circ \text{ V}$$

$$P_s = |E_s| \cdot |I_s| \cdot \cos(E_s \wedge I_s)$$

$$P_s = 1 \times 1.5992 \times 10^{-3} \times \cos(-1.5477)$$

$$P_s = 1.5986 \times 10^{-3} \text{ W}$$

$$\text{and } P_R = |E_R| \cdot |I_R| \cdot \cos(E_R \wedge I_R)$$

$$P_R = 0.1486 \times 7.43 \times 10^{-4} \cos(0)$$

$$P_R = 0.1486 \times 7.43 \times 10^{-4} \text{ W}$$

$$P_R = 1.1041 \times 10^{-4} \text{ W}$$

17. A generator of 1V, 1KHz, supplies power to a 100 Km open wire line terminated in 200 Ω resistance. The line parameters are $R = 10 \Omega/\text{Km}$, $L = 3.8\text{mH}/\text{Km}$, $G = 1 \times 10^{-6} \text{ mho}/\text{Km}$, $C = 0.0085 \mu\text{F}/\text{Km}$. Calculate the impedance, reflection coefficient, power and transmission efficiency.

[EC2305-APR/MAY 2011](16 Marks)

Solution:

Given: $E_g = 1\text{V}$, $f = 1000 \text{ Hz}$, $l = 100 \text{ Km}$, $Z_R = 200 \Omega$, $R = 10 \Omega/\text{Km}$, $L = 3.8\text{mH}/\text{Km}$, $G = 1 \times 10^{-6} \text{ mho}/\text{Km}$, $C = 0.0085 \mu\text{F}/\text{Km}$

$$\omega = 2\pi f = 2 \times 3.14 \times 1000 = 6280$$

The characteristic impedance is given by,

$$Z_o = \sqrt{\frac{Z}{Y}} = \sqrt{\frac{R + j\omega L}{G + j\omega C}}$$

$$Z = R + j\omega L = 10 + j(6280)(3.8 \times 10^{-3}) = 25.87 \angle 67.26^\circ$$

$$Y = G + j\omega C = 1 \times 10^{-6} + j(6280)(0.0085 \times 10^{-6}) = 5.339 \times 10^{-5} \angle 88.93^\circ$$

$$Z_o = \sqrt{\frac{25.87 \angle 67.26^\circ}{5.339 \times 10^{-5} \angle 88.93^\circ}}$$

$$Z_o = \frac{5.086}{7.307 \times 10^{-3}} \angle (67.26^\circ - 88.93^\circ) / 2$$

$$\mathbf{Z_o = 696.06 \angle -10.84^\circ \Omega}$$

The propagation constant is given by,

$$P = \gamma = \sqrt{ZY} = \sqrt{(R + j\omega L)(G + j\omega C)}$$

$$P = \gamma = \sqrt{25.87 \angle 67.26^\circ \times 5.339 \times 10^{-5} \angle 88.93^\circ}$$

$$P = \gamma = \sqrt{1.3812 \times 10^{-3} \angle (67.26^\circ + 88.93^\circ)}$$

$$P = \gamma = \alpha + j\beta = 0.03716 \angle 78.095^\circ \text{ (Or) } 7.6657 \times 10^{-3} + j0.03636$$

attenuation constant, $\alpha = 7.6657 \times 10^{-3}$ Np/Km

and phase constant, $\beta = 0.03636$ rad/Km

Reflection Coefficient, K

$$K = \frac{Z_R - Z_o}{Z_R + Z_o}$$

$$K = \frac{200 - 696.06 \angle -10.84^\circ}{200 + 696.06 \angle -10.84^\circ} = -0.557 + j0.0656 = 0.5609 \angle 173.28^\circ$$

$$\mathbf{K = 0.5609 \angle 173.28^\circ}$$

$$e^{\gamma l} = e^{(\alpha + j\beta)l} = e^{\alpha l} \angle \beta l = e^{(7.6657 \times 10^{-3})(100)} \angle (0.03636)(100)$$

$$e^{\gamma l} = e^{(7.6657 \times 10^{-3})(100)} \angle (0.03636)(100) \text{ rad}$$

$$e^{\gamma l} = e^{0.76657} \angle 208.3^\circ$$

$$\mathbf{e^{\gamma l} = 2.1524 \angle 208.3^\circ}$$

$$e^{-\gamma l} = e^{-(\alpha + j\beta)l} = e^{-\alpha l} \angle -\beta l = e^{-(7.6657 \times 10^{-3})(100)} \angle -(0.03636)(100)$$

$$e^{-\gamma l} = e^{-(7.6657 \times 10^{-3})(100)} \angle -(0.03636)(100) \text{ rad}$$

$$e^{-\gamma l} = e^{-0.76657} \angle -208.3^\circ$$

$$\mathbf{e^{-\gamma l} = 0.4646 \angle -208.3^\circ}$$

$$Z_s = Z_o \left\{ \frac{e^{\gamma l} + K e^{-\gamma l}}{e^{\gamma l} - K e^{-\gamma l}} \right\}$$

$$Z_s = 696.06 \angle -10.84^\circ \left\{ \frac{2.1524 \angle 208.3^\circ + (0.5609 \angle 173.28^\circ)(0.4646 \angle -208.3^\circ)}{2.1524 \angle 208.3^\circ - (0.5609 \angle 173.28^\circ)(0.4646 \angle -208.3^\circ)} \right\}$$

$$Z_s = 696.06 \angle -10.84^\circ \left\{ \frac{2.1524 \angle 208.3^\circ + 0.2606 \angle -35.02^\circ}{2.1524 \angle 208.3^\circ - 0.2606 \angle -35.02^\circ} \right\}$$

$$Z_S = 696.06 \angle -10.84^\circ \left\{ \frac{2.0487 \angle -145.17^\circ}{2.2813 \angle -157.56^\circ} \right\}$$

$$Z_S = 696.06 \angle -10.84^\circ \times 0.8980 \angle 12.39^\circ$$

$$\mathbf{Z_S = 625.08 \angle 1.548^\circ}$$

$$I_S = \frac{E_g}{Z_g + Z_{in}} = \frac{E_g}{Z_g + Z_S}$$

$$I_S = \frac{1}{0 + 625.08 \angle 1.548^\circ} = 1.5992 \times 10^{-3} \angle -1.548^\circ \text{ A}$$

$$\mathbf{I_S = 1.5992 \times 10^{-3} \angle -1.548^\circ}$$

$$E_S = I_S \times Z_S$$

$$E_S = 1.5992 \times 10^{-3} \angle -1.548^\circ \times 625.08 \angle 1.548^\circ$$

$$\mathbf{E_S = 1 \angle -3.4484 \times 10^{-4} \text{ V}}$$

We know that,

$$I = \frac{I_R}{2} \left(\frac{Z_R + Z_o}{Z_o} \right) \left[e^{\sqrt{ZY}s} - \frac{(Z_R - Z_o)}{(Z_R + Z_o)} e^{-\sqrt{ZY}s} \right]$$

At sending end, $s=1$, as s is measured from the receiving end.

$$I_S = \frac{I_R}{2} \left(\frac{Z_R + Z_o}{Z_o} \right) \left[e^{\sqrt{ZY}1} - K e^{-\sqrt{ZY}1} \right]$$

$$Z_R + Z_o = 893.28 \angle -8.427^\circ$$

$$K e^{\sqrt{ZY}1} = 0.5609 \angle 173.28^\circ \times 2.1524 \angle 208.3^\circ$$

$$K e^{\sqrt{ZY}1} = 1.2073 \angle 21.58^\circ$$

$$1.5992 \times 10^{-3} \angle -1.548^\circ = \frac{I_R}{2} \left(\frac{893.28 \angle -8.427^\circ}{696.06 \angle -10.84^\circ} \right) \left[2.1524 \angle 208.3^\circ - 1.2073 \angle 21.58^\circ \right]$$

$$1.5992 \times 10^{-3} \angle -1.548^\circ = \frac{I_R}{2} (1.2833 \angle 2.413^\circ) [3.354 \angle -154.11^\circ]$$

$$1.5992 \times 10^{-3} \angle -1.548^\circ = I_R \times 2.1523 \angle -151.70^\circ$$

$$\mathbf{I_R = 7.43 \times 10^{-4} \angle 150.15^\circ}$$

$$E_R = I_R \times Z_R = 7.43 \times 10^{-4} \angle 150.15^\circ \times 200 = 0.1486 \angle 150.153^\circ$$

$$\mathbf{E_R = 0.1486 \angle 150.15^\circ \text{ V}}$$

$$P_S = |E_S| \cdot |I_S| \cdot \cos(E_S \wedge I_S)$$

$$P_S = 1 \times 1.5992 \times 10^{-3} \times \cos(-1.5477)$$

$$\mathbf{P_S = 1.5986 \times 10^{-3} \text{ W}}$$

$$\text{and } P_R = |E_R| \cdot |I_R| \cdot \cos(E_R \wedge I_R)$$

$$P_R = 0.1486 \times 7.43 \times 10^{-4} \cos(0)$$

$$P_R = 0.1486 \times 7.43 \times 10^{-4} \text{ W}$$

$$P_R = 1.1041 \times 10^{-4} \text{ W}$$

$$\text{Transmission Efficiency, } \eta = \frac{P_R}{P_S} \times 100$$

$$\eta = \frac{1.1041 \times 10^{-4}}{1.5986 \times 10^{-3}} \times 100$$

$$\eta = 6.907 \%$$

18. A telephone cable 64 km long has a resistance of 13 Ω /km and a capacitance of 0.008 μf /km. Calculate the attenuation constant, velocity and wavelength of the line at 1000 Hz.

[EC2305-NOV/DEC 2016](6 Marks), [EC2305-MAY/JUN 2015](6 Marks), [EC2305-APR/MAY/JUN 2016](4 Marks)

Solution:

Given: $l=64\text{Km}$, $R=13 \Omega/\text{km}$, $C=0.008 \mu\text{f} / \text{km}$, $f=1000 \text{ Hz}$

$$\omega = 2\pi f = 2 \times 3.14 \times 1000 = 6280$$

The characteristic impedance is given by,

$$Z_o = \sqrt{\frac{R + j\omega L}{G + j\omega C}}$$

$$Z_o = \sqrt{\frac{13}{j(6280)(0.008 \times 10^{-6})}}$$

$$Z_o = \sqrt{\frac{13}{j5.024 \times 10^{-5}}} = \sqrt{\frac{13 \angle 0^\circ}{5.024 \times 10^{-5} \angle 90^\circ}}$$

$$Z_o = \frac{3.61}{7.088 \times 10^{-3}} \angle (0^\circ - 90^\circ) / 2$$

$$Z_o = 509.31 \angle -45^\circ$$

The propagation constant is given by,

$$P = \gamma = \sqrt{(R + j\omega L)(G + j\omega C)}$$

$$P = \gamma = \sqrt{(13) \times (j(6280)(0.008 \times 10^{-6}))}$$

$$P = \gamma = \sqrt{13 \times j5.024 \times 10^{-5}}$$

$$P = \gamma = \sqrt{6.5312 \times 10^{-4} \angle 90^\circ}$$

$$P = \gamma = \alpha + j\beta = 25.56 \times 10^{-3} \angle 45^\circ \text{ (Or) } 0.01807 + j0.01807$$

attenuation constant, $\alpha = 0.01807 \text{ Np/Km}$

and phase constant, $\beta = 0.01807 \text{ rad/Km}$

The velocity of propagation is given by,

$$v_p = \frac{\omega}{\beta}$$

$$v_p = \frac{6280}{0.01807} = 3.48 \times 10^5 \text{ Km/sec}$$

$$\lambda = \frac{2\pi}{\beta} = \frac{2\pi}{0.01807} = 347.54 \text{ m}$$

19. A transmission line has $L = 10 \text{ mH/m}$, $C = 10^{-7} \text{ F/m}$, $R = 20 \Omega/\text{m}$ and $G = 10^{-5} \text{ mho/m}$. Find the input impedance at a frequency of $\left(\frac{5000}{2\pi}\right) \text{ Hz}$, if the line is very long. **[EC2305-NOV/DEC 2013] (6 Marks)**

Solution:

Given: $L = 10 \text{ mH/m}$, $C = 10^{-7} \text{ F/m}$, $R = 20 \Omega/\text{m}$ and $G = 10^{-5} \text{ mho/m}$,

$$f = \left(\frac{5000}{2\pi}\right)$$

$$\omega = 2\pi f = 2\pi \times \left(\frac{5000}{2\pi}\right) = 5000$$

The characteristic impedance is given by,

$$Z_o = \sqrt{\frac{R + j\omega L}{G + j\omega C}}$$

$$Z_o = \sqrt{\frac{20 + j(5000)(10 \times 10^{-3})}{10^{-5} + j(5000)(10 \times 10^{-7})}}$$

$$Z_o = \sqrt{\frac{20 + j50}{10^{-5} + j5 \times 10^{-4}}} = \sqrt{\frac{53.85 \angle 68.199^\circ}{5.0 \times 10^{-4} \angle 88.85^\circ}}$$

$$Z_o = \frac{7.338}{0.0224} \angle (68.199^\circ - 88.85^\circ) / 2$$

$$\mathbf{Z_o = 327.59 \angle -10.33^\circ \Omega}$$

20. The characteristic impedance of a uniform transmission line is 2309.6 ohms at a frequency of 800 Hz . At this frequency, the propagation constant is $0.054(0.0366 + j0.99)$. Determine R and L .

[EC2305-NOV/DEC 2013] (6 Marks), [EC2305-NOV/DEC 2010] (6 Marks)

Solution:

Given: $Z_o = 2309.6 \Omega$, $f = 800 \text{ Hz}$, $P = \gamma = 0.054(0.0366 + j0.99) = 0.054 \angle 87.9^\circ$

$$\omega = 2\pi f = 2 \times 3.14 \times 800 = 5024$$

$$\begin{aligned} R = j\omega L = Z_o P &= 2309.6 \times 0.054 \angle 87.9^\circ \\ &= 4.57 + j124.63 \end{aligned}$$

Comparing real and imaginary terms,

$$\mathbf{R = 4.57\ ohms/Km}$$

$$\omega L = 124.63$$

$$L = \frac{124.63}{5024} = 0.0248\text{ H/Km (Or) } 24.8\text{ mH/Km}$$

$$\mathbf{L=24.8\ mH/Km}$$

21. A transmission line has the following per unit length parameters: $L=0.1\mu\text{H}$, $R=5\Omega$, $C=300\text{pF}$ and $G=0.01\text{mhos}$. Calculate the propagation constant and characteristic impedance at 500 MHz. **[EC2305-NOV/DEC 2010] (8 Marks)**

Solution:

Given: $f=500\text{MHz}$, $R = 5\ \Omega$, $L = 0.1\mu\text{H}$, $G = 0.01\ \text{mho}$, $C = 300\ \text{pF}$

$$\omega = 2\pi f = 2 \times 3.14 \times 500 \times 10^6 = 3140 \times 10^6$$

The characteristic impedance is given by,

$$Z_o = \sqrt{\frac{Z}{Y}} = \sqrt{\frac{R + j\omega L}{G + j\omega C}}$$

$$Z = R + j\omega L = 5 + j(3140 \times 10^6)(0.1 \times 10^{-6}) = 314.04 \angle 89.09^\circ$$

$$Y = G + j\omega C = 0.01 + j(3140 \times 10^6)(300 \times 10^{-12}) = 0.9421 \angle 89.39^\circ$$

$$Z_o = \sqrt{\frac{314.04 \angle 89.09^\circ}{0.9421 \angle 89.39^\circ}}$$

$$Z_o = \frac{17.721}{0.9706} \angle (89.09^\circ - 89.39^\circ) / 2$$

$$\mathbf{Z_o = 18.258 \angle -0.15^\circ \Omega}$$

The propagation constant is given by,

$$P = \gamma = \sqrt{ZY} = \sqrt{(R + j\omega L)(G + j\omega C)}$$

$$P = \gamma = \sqrt{314.04 \angle 89.09^\circ \times 0.9421 \angle 89.39^\circ}$$

$$P = \gamma = \sqrt{295.86 \angle (89.09^\circ + 89.39^\circ)}$$

$$P = \gamma = \alpha + j\beta = 17.2 \angle 89.24^\circ \text{ (Or) } 0.2281 + j17.198$$

22. A transmission line has the following constants $R = 10.4 \Omega/\text{km}$, $L = 3.666 \text{ mH}/\text{km}$, $G = 0.08 \times 10^{-6} \text{ mho}/\text{km}$ and $C = 0.00835 \mu\text{F}/\text{km}$. Calculate its characteristic impedance, attenuation, phase constant and phase velocity.
[EC2305-MAY/JUN 2012](8 Marks)

Solution:

Given: $R = 10.4 \Omega/\text{km}$, $L = 3.666 \text{ mH}/\text{km}$, $G = 0.08 \times 10^{-6} \text{ mho}/\text{km}$ and $C = 0.00835 \mu\text{F}/\text{km}$

Let $f = 1000 \text{ Hz}$,

$$\omega = 2\pi f = 2 \times 3.14 \times 1000 = 6280$$

The characteristic impedance is given by,

$$Z_o = \sqrt{\frac{Z}{Y}} = \sqrt{\frac{R + j\omega L}{G + j\omega C}}$$

$$Z = R + j\omega L = 10.4 + j(6280)(3.666 \times 10^{-3}) = 25.263 \angle 65.69^\circ$$

$$Y = G + j\omega C = 0.08 \times 10^{-6} + j(6280)(0.00835 \times 10^{-6}) = 5.244 \times 10^{-5} \angle 89.91^\circ$$

$$Z_o = \sqrt{\frac{25.263 \angle 65.69^\circ}{5.244 \times 10^{-5} \angle 89.91^\circ}}$$

$$Z_o = \frac{5.0262}{7.242 \times 10^{-3}} \angle (65.69^\circ - 89.91^\circ) / 2$$

$$\mathbf{Z_o = 694.08 \angle -12.11^\circ \Omega}$$

The propagation constant is given by,

$$P = \gamma = \sqrt{ZY} = \sqrt{(R + j\omega L)(G + j\omega C)}$$

$$P = \gamma = \sqrt{25.263 \angle 65.69^\circ \times 5.244 \times 10^{-5} \angle 89.91^\circ}$$

$$P = \gamma = \sqrt{1.3248 \times 10^{-3} \angle (65.69^\circ + 89.91^\circ)}$$

$$\mathbf{P = \gamma = \alpha + j\beta = 0.0364 \angle 77.8^\circ \text{ (Or) } 7.6922 \times 10^{-3} + j0.0356}$$

attenuation constant, $\alpha = 7.6922 \times 10^{-3} \text{ Np/Km}$

phase constant, $\beta = 0.0356 \text{ rad/Km}$

$$\text{Phase Velocity, } v_p = \frac{\omega}{\beta} = \frac{6280}{0.0356} = 1.76 \times 10^5 \text{ Km/sec}$$

23. A telephone line has $R=6\Omega/\text{Km}$, $L=2.2\text{mH}/\text{Km}$, $C=0.005\mu\text{F}/\text{Km}$ and $G=0.05\times 10^{-6}\text{ mho}/\text{Km}$. Determine the characteristic impedance and propagation constant at 1 KHz. **[EC2305-APR/MAY 2016] (6 Marks)**

Solution:

Given: $R = 6 \Omega/\text{km}$, $L = 2.2 \text{ mH}/\text{km}$, $G = 0.05 \times 10^{-6} \text{ mho}/\text{km}$ and $C = 0.005 \mu\text{F}/\text{km}$, $f = 1000 \text{ Hz}$,

$$\omega = 2\pi f = 2 \times 3.14 \times 1000 = 6280$$

The characteristic impedance is given by,

$$Z_o = \sqrt{\frac{Z}{Y}} = \sqrt{\frac{R + j\omega L}{G + j\omega C}}$$

$$Z = R + j\omega L = 6 + j(6280)(2.2 \times 10^{-3}) = 15.063 \angle 66.53^\circ$$

$$Y = G + j\omega C = 0.05 \times 10^{-6} + j(6280)(0.005 \times 10^{-6}) = 3.14 \times 10^{-5} \angle 89.91^\circ$$

$$Z_o = \sqrt{\frac{15.063 \angle 66.53^\circ}{3.14 \times 10^{-5} \angle 89.91^\circ}}$$

$$Z_o = \frac{3.881}{5.604 \times 10^{-3}} \angle (66.53^\circ - 89.91^\circ) / 2$$

$$\mathbf{Z_o = 692.59 \angle -11.69^\circ \Omega}$$

The propagation constant is given by,

$$P = \gamma = \sqrt{ZY} = \sqrt{(R + j\omega L)(G + j\omega C)}$$

$$P = \gamma = \sqrt{15.063 \angle 66.53^\circ \times 3.14 \times 10^{-5} \angle 89.91^\circ}$$

$$P = \gamma = \sqrt{0.473 \times 10^{-3} \angle (66.53^\circ + 89.91^\circ)}$$

$$\mathbf{P = \gamma = \alpha + j\beta = 0.0217 \angle 78.22^\circ \text{ (Or) } 4.43 \times 10^{-3} + j0.0212}$$

attenuation constant, $\alpha = 4.43 \times 10^{-3} \text{ Np}/\text{Km}$

phase constant, $\beta = 0.0212 \text{ rad}/\text{Km}$

24. A cable has the following parameters: $R=48.75 \text{ ohm}/\text{Km}$, $L=1.09\text{mH}/\text{Km}$, $G=38.75\mu\text{mho}/\text{Km}$, $C=0.059 \mu\text{F}/\text{Km}$. Determine the characteristic impedance, propagation constant and wavelength for a source of $f=1600\text{Hz}$ and $E_s=1\text{V}$. **[EC2305-APR/MAY 2013](6 Marks)**

Solution:

Given: $R=48.75 \text{ ohm}/\text{Km}$, $L=1.09\text{mH}/\text{Km}$, $G=38.75\mu\text{mho}/\text{Km}$, $C=0.059 \mu\text{F}/\text{Km}$

$$\omega = 2\pi f = 2 \times 3.14 \times 1600 = 10048$$

The characteristic impedance is given by,

$$Z_o = \sqrt{\frac{Z}{Y}} = \sqrt{\frac{R + j\omega L}{G + j\omega C}}$$

$$Z = R + j\omega L = 48.75 + j(10048)(1.09 \times 10^{-3}) = 49.965 \angle 12.66^\circ$$

$$Y = G + j\omega C = 38.75 \times 10^{-6} + j(10048)(0.059 \times 10^{-6}) = 5.941 \times 10^{-4} \angle 86.26^\circ$$

$$Z_o = \sqrt{\frac{49.965 \angle 12.66^\circ}{5.941 \times 10^{-4} \angle 86.26^\circ}}$$

$$Z_o = \frac{7.069}{0.0244} \angle (12.66^\circ - 86.26^\circ) / 2$$

$$\mathbf{Z_o = 290.02 \angle -36.8^\circ \Omega}$$

The propagation constant is given by,

$$P = \gamma = \sqrt{ZY} = \sqrt{(R + j\omega L)(G + j\omega C)}$$

$$P = \gamma = \sqrt{49.965 \angle 12.66^\circ \times 5.941 \times 10^{-4} \angle 86.26^\circ}$$

$$P = \gamma = \sqrt{0.02968 \angle (12.66^\circ + 86.26^\circ)}$$

$$P = \gamma = \alpha + j\beta = 0.1723 \angle 49.46^\circ \text{ (Or) } 0.112 + j0.131$$

attenuation constant, $\alpha = 0.112 \text{ Np/Km}$

and phase constant, $\beta = 0.131 \text{ rad/Km}$

Wavelength is given by,

$$\lambda = \frac{2\pi}{\beta} = \frac{2\pi}{0.131} = 47.96 \text{ m}$$
